

**Shri Ramdeobaba College of Engineering and Management,
Nagpur-13.**

**Department of Electronics Engineering
ENP352 –CMOS Digital Circuit Design Lab**

Lab 3

Effect of trans-conductance ratios on VTC of CMOS inverter and
simulation of the Intrinsic Propagation delay of inverter.

Odd Semester – 2023-24



Name:	Harsh Misha
Batch / Roll No.	A2-22
Semester/Section:	V th A
Date of Performance:	21/10/23
Date of Submission:	28/10/23
Name & Signature of Faculty	Prof Prachi Rane

Lab-03

1) **Aim:** Investigate using SPICE and the long-channel CMOS process parameters supplied to you, the transfer curves for the CMOS inverter with trans-conductance ratios β_n/β_p 3, 1, and 1/3. Explain what changing the ratio does to the transfer characteristics. Estimate and simulate the intrinsic propagation delays of inverter if short channel devices are used (PMOS: NMOS=2:1).

✓ **Software Used:** LTspice

✓ **Circuit Diagram:**

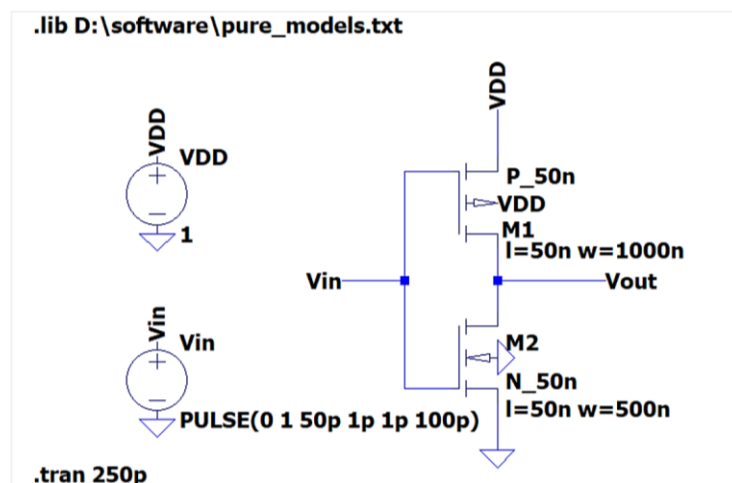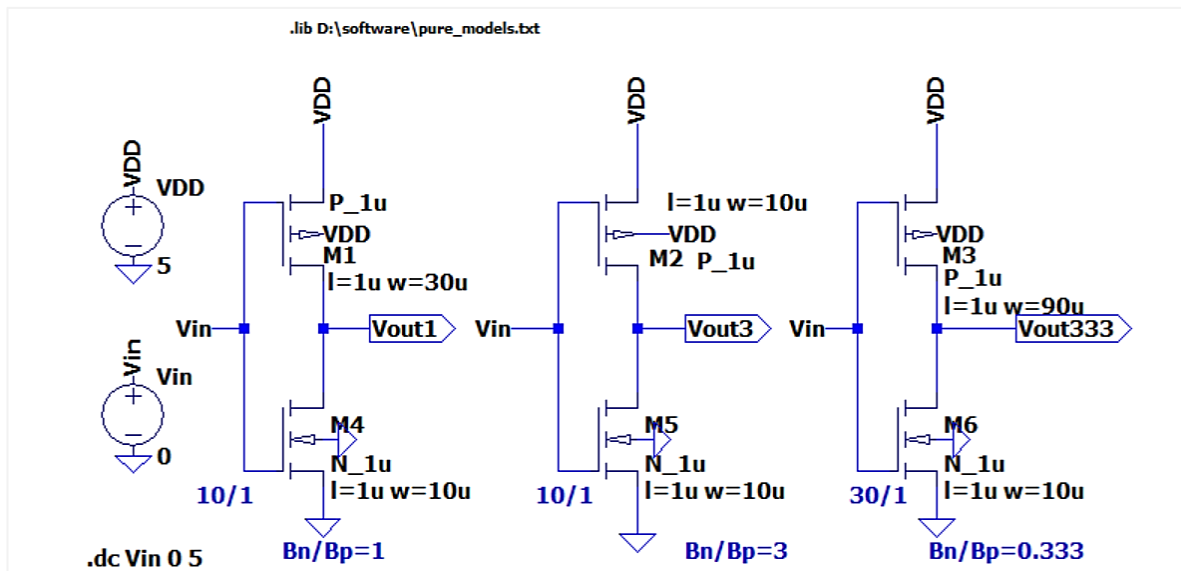

✓ **Observation Table**

Table No. 1: For Inverter (Long Channel) ($W_n=10\mu$ $L_n=1\mu$) ($W_p=30\mu$ $L_p=1\mu$)

Value of β_n/β_p	Switching Threshold of the inverter (V_m)
$\beta_n/\beta_p= 1$	2.558V
Value of β_n/β_p	Switching Threshold of the inverter (V_m)
$\beta_n/\beta_p= 1/3$	3.122V
Value of β_n/β_p	Switching Threshold of the inverter (V_m)
$\beta_n/\beta_p= 3$	1.905V

Table No. 2: For Inverter (Short Channel) (Wn=50n Ln=500n) (Wp=50n Lp=1000n)

Variables	Values
t_{PHL}	$59.66ps - 50.5ps = 9.16ps$
t_{PLH}	$160.99ps - 151.49ps = 9.50ps$

✓ **Calculations:**

Theoretical $V_m = V_{DD}/2 = 5/2 = 2.5V$

For T_{PHL} :

$V_{in} = 50.5ps$

$V_{out} = 59.66ps$

For T_{PLH} :

$V_{in} = 151.49ps$

$V_{out} = 160.99ps$

Propagation Delay

$T_{PLH} = V_{out} - V_{in}$

$= 59.66ps - 50.5ps$

$= 9.16ps$


Propagation Delay

$T_{PLH} = V_{out} - V_{in}$


$= 160.99ps - 151.49ps$

$= 9.50ps$

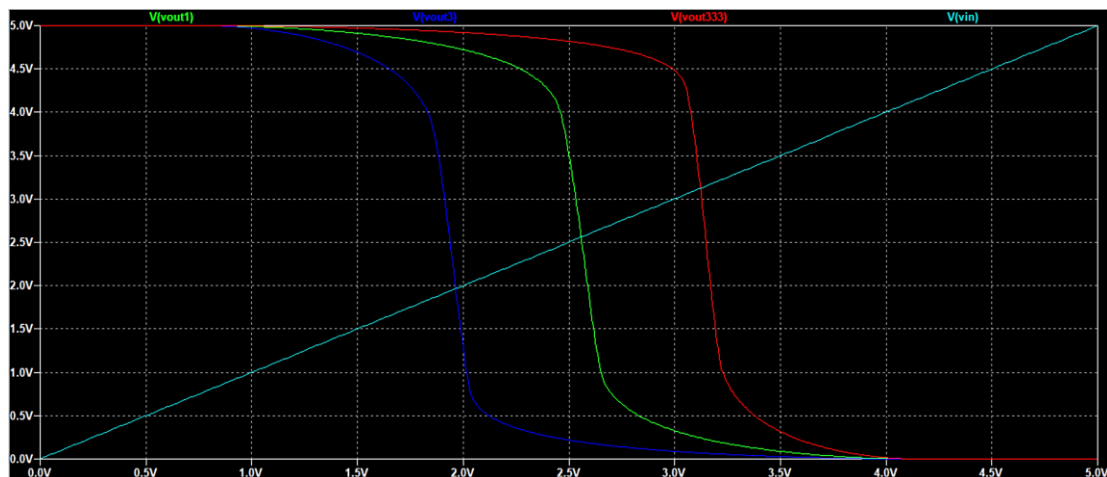✓ **Obtained Waveforms/Simulation Results:**



Delay For Symmetric Inverter:

 

✓ Discussion and Conclusion:

For a long-channel inverter with a B_n/B_p ratio of 1, the switching threshold is 2.55 V. This threshold is where V_{in} equals V_{out} on the transfer curve, and with a ratio of 1, both nmos and pmos transistors have equal strength. If we change the ratio to 0.33, the pmos becomes stronger, shifting its VTC to the left. This occurs because the input voltage that triggers an output change moves to lower levels. Conversely, if we make the nmos stronger (ratio $B_n/B_p=3$), the VTC shifts to the right, making the inverter less sensitive to lower input voltages, and the transition from low to high occurs at a higher input voltage. The propagation delay of a logic gate is approximately 9.1 ps for both t_{PHL} (low to high transition) and t_{PLH} (high to low transition), calculated at the 50% point of the input-output transition.

Batch-A2 -22_Lab-03