

Shri Ramdeobaba College of Engineering and Management, Nagpur-13.

Department of Electronics Engineering

ENP352 –CMOS Digital Circuit Design Lab

Odd Semester – 2023-24

Lab 05

Driving Big Capacitive Loads.


Name:	Harsh Mishra
Batch / Roll No.	A2/22
Semester/Section:	5/A
Date of Performance:	28/10/2023
Date of Submission:	30/10/2023
Name & Signature of Faculty	Prof. P. Rane

Lab-05

- 1) **Aim:** Design a buffer (chain of inverters) to drive the load capacitance with a minimum delay. You need to start the design from the minimum sized inverter ($L=L_n=L_p=50n$, $W_p=450n$, $W_n=150n$). Load that needs to be driven is of 1 pF . (Use short channel models).

✓ **Software Used: LTspice**

✓ **Circuit Diagram:**

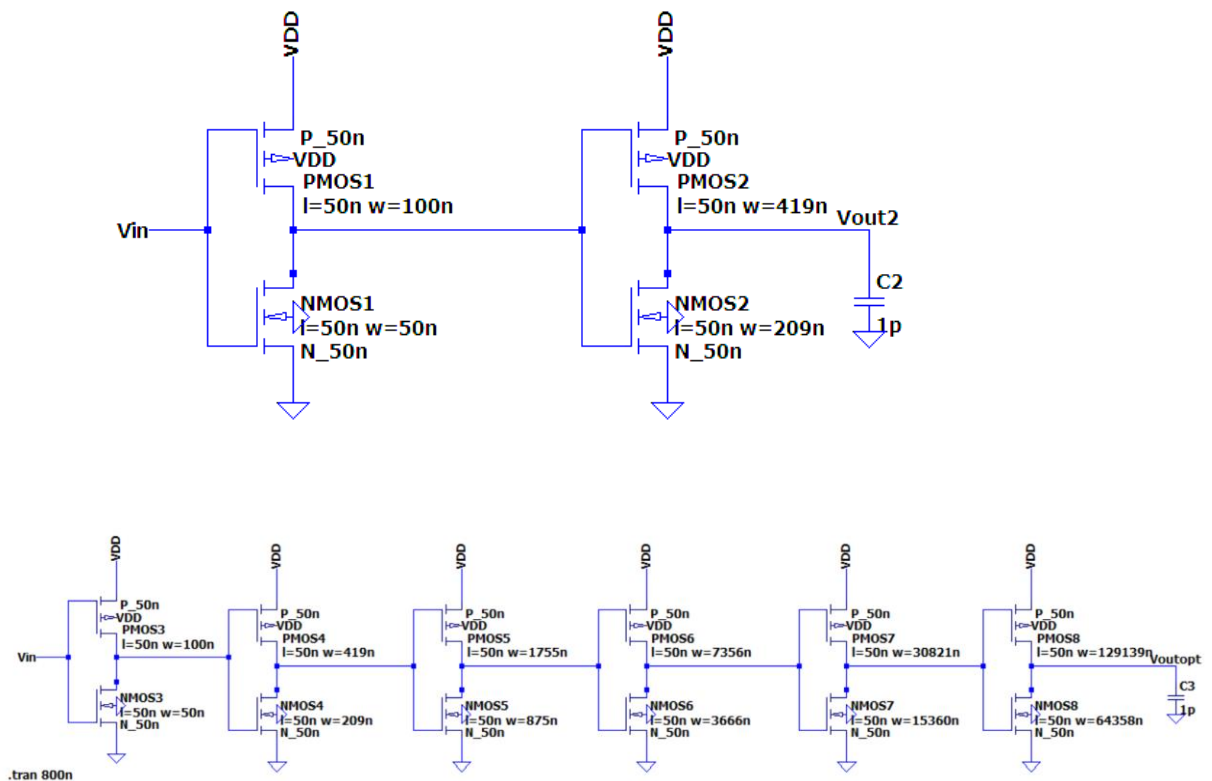

✓ **Observation Table**

Table No. 1: For chain of inverters (Short Channel)

Optimal no. of stages: 06

Observed delay from input to output:

Stage	W/L (NMOS)	W/L (PMOS)
#1	(W=50n; L=50n)	(W=100n ;L=50n)
#2	(W=209n; L=50n)	(W=419n ;L=50n)
#3	(W=875n; L=50n)	(W=1755n ;L=50n)
#4	(W=3666n; L=50n)	(W=7356n ;L=50n)
#5	(W=15360n; L=50n)	(W=30821n ;L=50n)
#6	(W=64358n; L=50n)	(W=129139n ;L=50n)
#7	(W=269660n; L=50n)	(W=541092n; L=50n)
#8	(W=1128527n; L=50n)	(W=2264470n; L=50n)

Table No. 2: For chain of inverters (Short Channel)

No. of stages: 01

Observed delay from input to output: 20.42n

Table No. 3: For chain of inverters (Short Channel)

No. of stages: 02

Observed delay from input to output: 4.12n

Table No.4: For chain of inverters (Short Channel)

No. of stages: 03

Observed delay from input to output: 1.14n

Table No.5 For chain of inverters (Short Channel)

No. of stages: 04

Observed delay from input to output: 0.427n

Table No.6: For chain of inverters (Short Channel)

No. of stages: 05

Observed delay from input to output: 0.414n

Table No.7: For chain of inverters (Short Channel)

No. of stages: 06

Observed delay from input to output: 0.34n

Table No.8: For chain of inverters (Short Channel)

No. of stages: 07

Observed delay from input to output: 0.74n

✓ Calculations:

Case 1 (single stage):

$$t1=400n$$

$$t2=420.42n$$

$$\begin{aligned}t_{phl} &= 420.42n - 420n \\ &= 20.42n\end{aligned}$$

$$t1=500n$$

$$t2=520.42n$$

$$\begin{aligned}t_{plh} &= 520.42n - 500n \\ &= 20.42n\end{aligned}$$

$$T_{pd} = (t_{plh} + t_{phl})/2$$

$$= 20.42n$$

Case 2 (stages=2):

$$t1=500n$$

$$t2=504.12n$$

$$\begin{aligned} t_{phl} &= 500n - 504.12n \\ &= 4.12n \end{aligned}$$

$$t1=400n$$

$$t2=404.12n$$

$$\begin{aligned} t_{plh} &= 404.12n - 400n \\ &= 4.12n \end{aligned}$$

$$\begin{aligned} T_{pd} &= (t_{plh} + t_{phl})/2 \\ &= 4.12n \end{aligned}$$

Case 3 (stages=3):

$$t1=400n$$

$$t2=401.14n$$

$$\begin{aligned} t_{phl} &= 401.14n - 400n \\ &= 1.14n \end{aligned}$$

$$t1=500n$$

$$t2=501.14n$$

$$\begin{aligned} t_{plh} &= 501.14n - 500n \\ &= 1.14n \end{aligned}$$

$$\begin{aligned} T_{pd} &= (t_{plh} + t_{phl})/2 \\ &= 1.14n \end{aligned}$$

Case 4 (stages=4):

$$t1=500n$$

$$t2=500.427n$$

$$t_{phl} = 500.427n - 500n$$

$$= 0.427n$$

$$t_1 = 400n$$

$$t_2 = 400.427n$$

$$t_{plh} = 400.427n - 400n$$

$$= 0.427n$$

$$T_{pd} = (t_{plh} + t_{phl})/2$$

$$= 0.427n$$

Case 5 (stages=5):

$$t_1 = 400n$$

$$t_2 = 400.414n$$

$$t_{phl} = 400.414n - 400n$$

$$= 0.414n$$

$$t_1 = 500n$$

$$t_2 = 500.41n$$

$$t_{plh} = 500.41n - 500n$$

$$= 0.41n$$

$$T_{pd} = (t_{plh} + t_{phl})/2$$

$$= 0.41n$$

Case 6 (stages=6):

$$t_1 = 500n$$

$$t_2 = 500.35n$$

$$t_{phl} = 500.35n - 500n$$

$$= 0.35n$$

$$t_1 = 400n$$

$$t_2 = 400.33n$$

$$t_{plh} = 400.33n - 400n$$

$$= 0.33n$$

$$T_{pd} = (t_{plh} + t_{phl})/2$$

$$= 0.34n$$

Case 7 (stages=7):

$$t1=500n$$

$$t2=500.76n$$

$$\begin{aligned}tphl &= 500.76n - 500n \\ &= 0.76n\end{aligned}$$

$$t1=400n$$

$$t2=400.73n$$

$$\begin{aligned}tplh &= 400.73n - 400n \\ &= 0.73n\end{aligned}$$

$$\begin{aligned}Tpd &= (tplh+tphl)/2 \\ &= 0.74n\end{aligned}$$

Case 8 (stages=8):

$$t1=300n$$

$$t2=300.35n$$

$$\begin{aligned}tphl &= 300.34n - 300n \\ &= 0.34n\end{aligned}$$

$$t1=200n$$


$$t2=200.32n$$

$$\begin{aligned}tplh &= 200.32n - 200n \\ &= 0.32n\end{aligned}$$


$$\begin{aligned}Tpd &= (tplh+tphl)/2 \\ &= 0.33n\end{aligned}$$

Obtained Waveforms/Simulation Results:

Case2: (stages = 2)

 

Case6:(Stages=6)

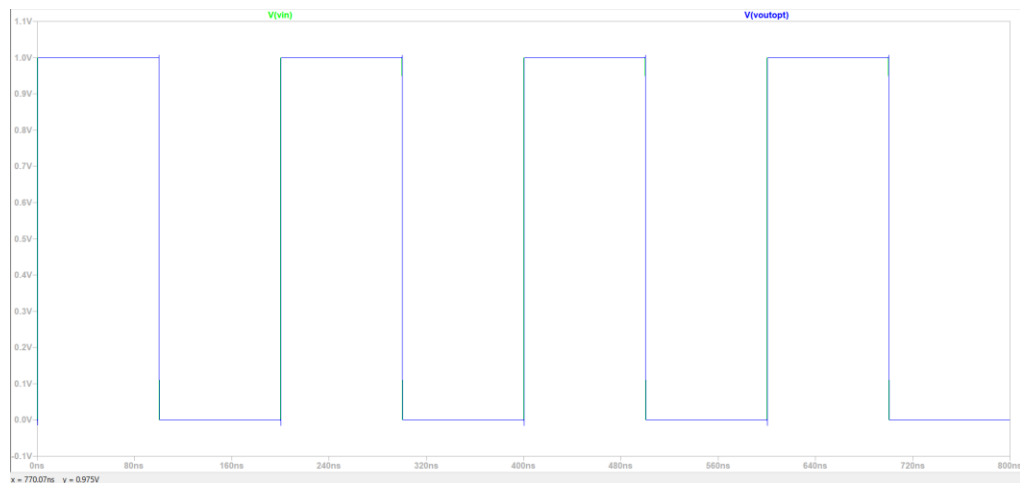

✓ Discussion and Conclusion:

As the number of stages of inverters is increased the propagation delay is reduced drastically due to the increase in fanout at each stage. We take one stage less than the optimal value of n since after a certain point the reduction in delay is not that significant but the size increases very significantly, therefore avoid to go for the optimal value.

Batch-A2 _22-Lab-No-5