# Shri Ramdeobaba College of Engineering and Management, Nagpur-13.

# **Department of Electronics Engineering**

# ENP402 - CMOS VLSI Design Lab

**Odd Semester – 2023-24** 

#### <u>Lab 01</u>

Evaluate the output characteristics for 1um (long channel) and 50nm (short channel)

technology N-channel and P-channel MOSFET.

Name:	Harsh Devendra Mishra
Batch / Roll No.	A2_22
Semester/Section:	Sem V-A
Date of Performance:	09/09/23
<b>Date of Submission:</b>	16/09/23
Name & Signature of Faculty	P. P. Rane

# **Lab-01**

**Aim:** Evaluate the output characteristics for 1um (long channel) and 50nm (short channel) technology N-channel and P-channel MOSFET

**✓** Software Used: LTspice

## **✓** Circuit Diagram:

#### **Nmos:**

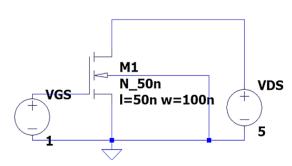


Fig 1.0 Nmos short channel

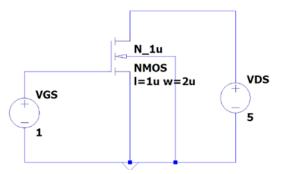


Fig 2.0 Nmos long channel

#### **Pmos:**

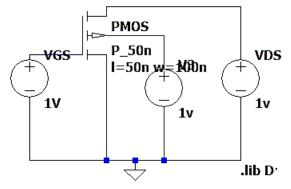


Fig 3.0 Pmos short channel

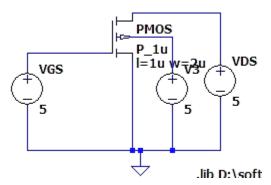


Fig 4.0 Pmos long channel

**Table No. 1: For NMOS (Long Channel)** 

W/L	Rds.	Region of operation
(W= 2u L= 1u)	73k	Linear
(W=2u L= 1u)	205k	Saturation

**Table No. 2: For PMOS (Long Channel)** 

(W= 2u L= 1u)	11.87k	Linear
(W= 2u L= 1u)	39.23k	Saturation

## **Table No. 3: For NMOS (Short Channel)**

(W= 100n L= 50n)	21.64k	Linear
(W= 100n L= 50n)	121.60k	Saturation

## **Table No. 4: For PMOS (Short Channel)**

(W= 100n L= 50n)	26.33k	Linear
(W= 100n L= 50n)	28.76k	Saturation

#### **✓** Calculations:

• The formula used to calculate **Rds** is =  $(slope)^{-1}$ 

### **✓** Obtained Waveforms/Simulation Results:

#### **Nmos:**

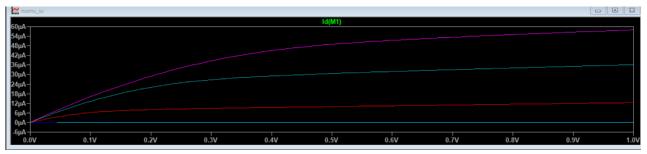


Fig 1.1 Nmos short channel

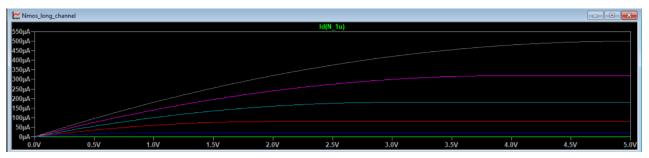


Fig 2.1 Nmos short channel

# **Pmos:**

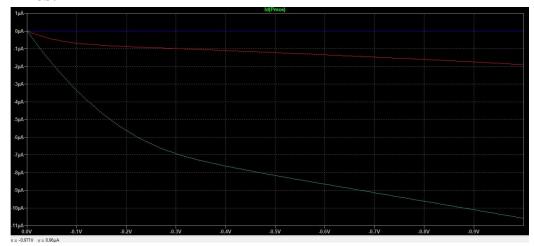


Fig 3.1 Pmos short channel

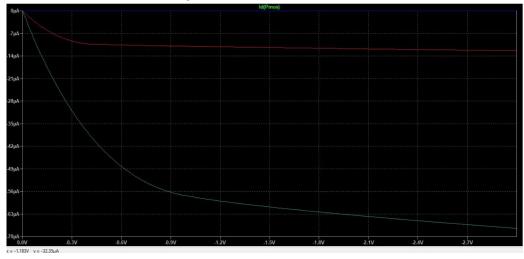


Fig 4.1 Pmos long channel

# **✓** Discussion and Conclusion:

o Linear Region: Vds<Vgs-Vt

o Saturation Region: Vds>=Vgs-Vt

Value of output resistance is more in saturation region and less in linear region for both Nmos and Pmos.

Batch\_A2-22\_Lab-No- 01