

Shri Ramdeobaba College of Engineering and Management, Nagpur-13.
Department of Electronics Engineering
ENP352 –CMOS Digital Circuit Design Lab
Odd Semester – 2023-24

Lab 06

Sequential Logic Element

Name:	Harsh Devendra Mishra
Batch / Roll No.	A2-26
Semester/Section:	Sem V·A
Date of Performance:	18/11/23
Date of Submission:	25/11/23
Name & Signature of Faculty	P. Prachi Rane


Lab-06

1) **Aim:** Implement D F/F. Define and estimate setup time for your design through SPICE simulation.


✓ **Software Used:** LT Spice

✓ **Circuit Diagram:**


D Flip-Flop

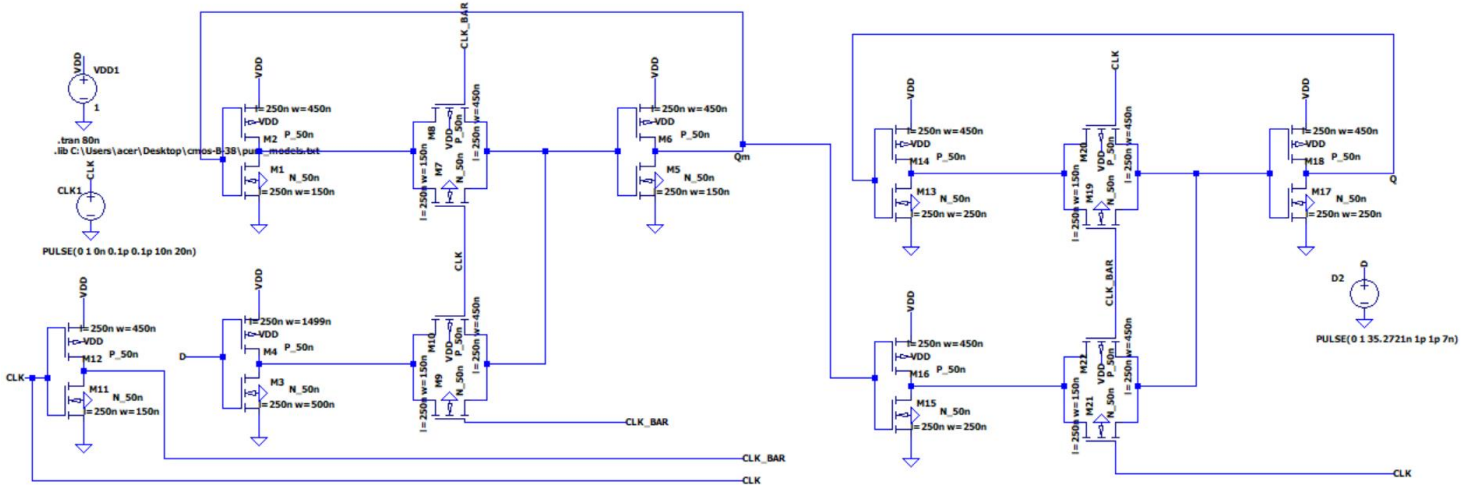

Positive Latch

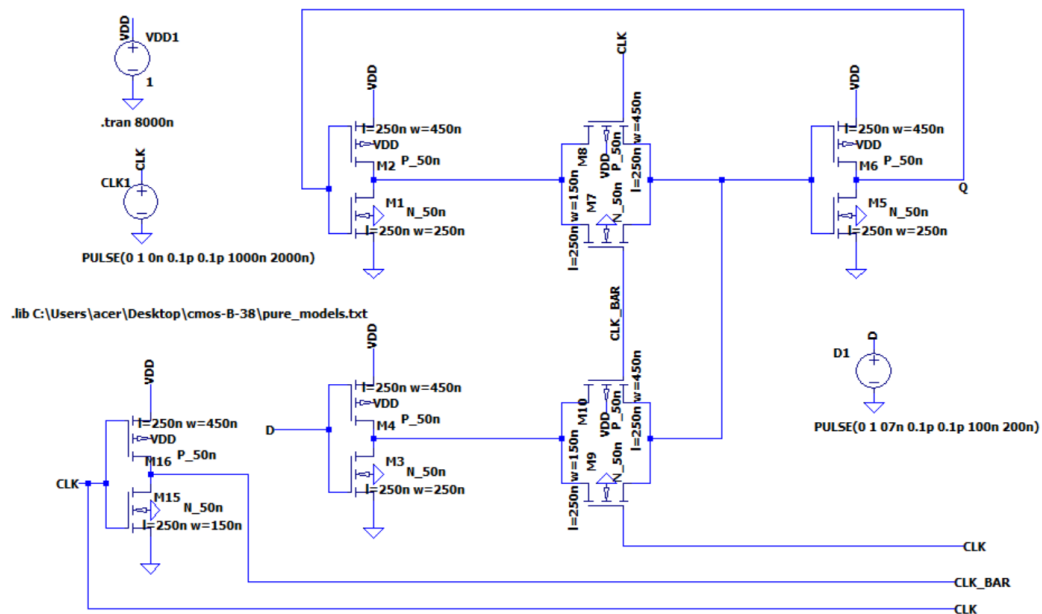

Negative Latch:

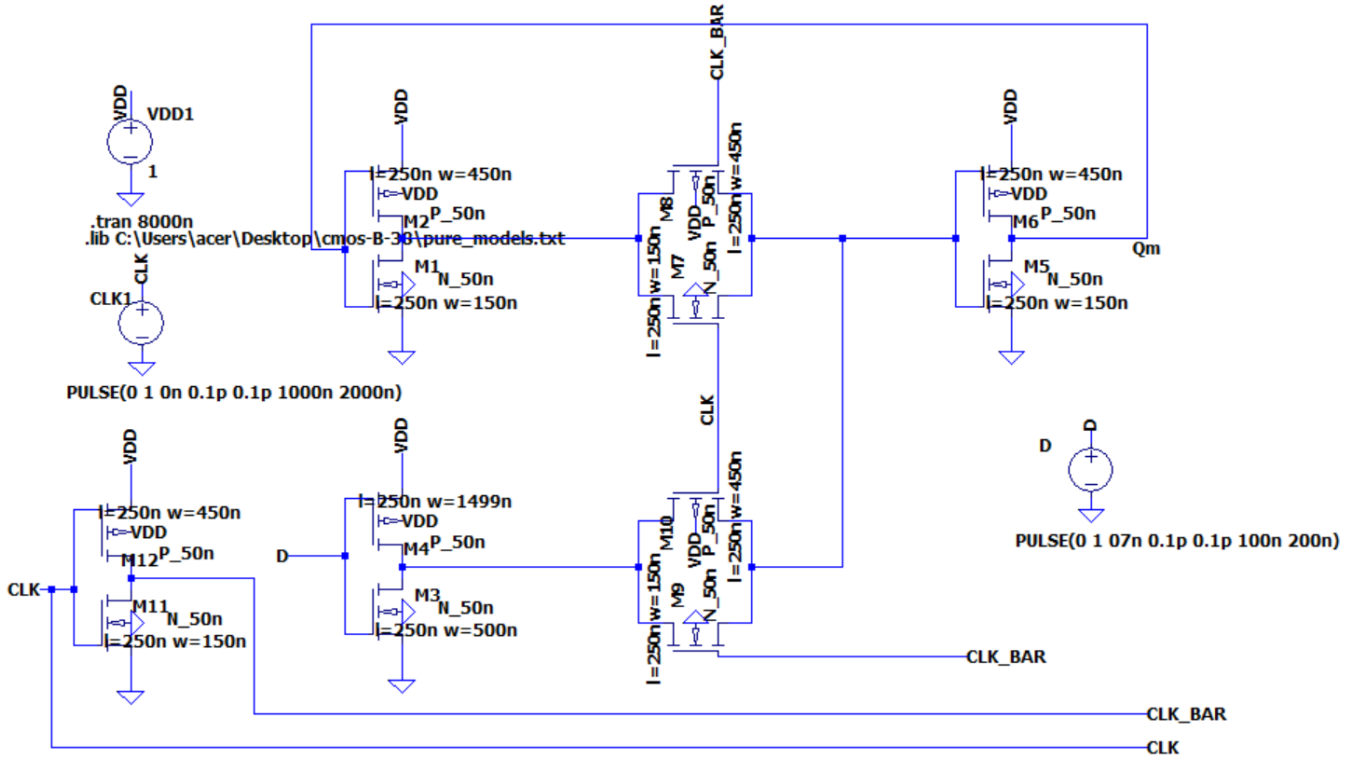

✓ Observation

Table No. 1: DFF (Short Channel)

Observed delay from input to output:

	Relative position (separation) of CLK and D (ns)	T_{c-t-q} (ns)	Set-up time of the design (T_{SU}) (ns)
Case 1	2.9883	$0.8994(LH)+1.0881(HL)=0.99375$	Setup Time =4.1712
Case 2	3.4864	$0.8864(LH)+1.086(HL)=0.9862$	
Case 3	3.857	$0.891(LH)+1.0878(HL)=0.9894$	
Case 4	3.8599	$0.895(LH)+1.0921(HL)=0.9935$	
Case 5	3.9844	$0.8901(LH)+1.0869(HL)=0.9885$	
Case 6	4.1712	$0.8902(LH)+1.0929(HL)=0.9915$	

✓ Calculations:

Case 1

$$T_{PHL} = 61.0907 - 60.0026 = 1.0881\text{ns}$$

$$T_{PLH} = 40.8892 - 39.9898 = 0.8994\text{ns}$$

$$T_{PD} = 0.99375\text{ns}$$

Case 2

$$T_{PHL} = 61.0885 - 60.0025 = 1.086\text{ns}$$

$$T_{PLH} = 40.8882 - 40.0018 = 0.8864\text{ns}$$

$$T_{PD} = 0\text{ns}$$

Case 3

$$T_{PHL} = 61.091 - 60.0032 = 1.0878\text{ns}$$

$$T_{PLH} = 40.891 - 40 = 0.891\text{ns}$$

$$T_{PD} = 0.9894\text{ns}$$

Case 4

$$T_{PHL} = 61.092 - 60.0016 = 1.0920\text{ns}$$

$$T_{PLH} = 40.87 - 39.98 = 0.892\text{ns}$$

$$T_{PD} = 0.985\text{ns}$$

Case 5

$$T_{PHL} = 61.0938 - 60.00164 = 1.0921\text{ns}$$

$$T_{PLH} = 40.891 - 39.9960 = 0.895\text{ns}$$

$$T_{PD} = 0.9935\text{ns}$$

Case 6:


$$T_{PHL} = 61.0943 - 60.0014 = 1.0929\text{ns}$$

$$T_{PLH} = 40.8873 - 39.9971 = 0.8902\text{ns}$$


$$T_{PD} = 0.9862\text{ns}$$

✓ Obtained Waveforms/Simulation Results:


D Flip-Flop:

 

Positive Latch:

 

Negative Latch:

 

✓ Discussion and Conclusion:

From this experiment, we successfully analyze and understand the behavior of the D flip-flop in digital sequential circuit and determine the time required for the input signal to settle before the clock edge arrivals which is known as setup time. In D flip-flop as the distance between clock and D input increases by some parameters than it gives better output.

Batch_A2-22_Lab-No- 06